

## 11.2 Transistor biasing

It has already been discussed that for faithful amplification, a transistor amplifier must satisfy three basic conditions, namely : (i) proper zero signal collector current, (ii) proper base-emitter voltage at any instant and (iii) proper collector-emitter voltage at any instant. It is the fulfilment of these conditions which is known as transistor biasing.

[The proper flow of zero signal collector current and the maintenance of proper collector-emitter voltage during the passage of signal is known as **transistor biasing**.

The basic purpose of transistor biasing is to keep the base-emitter junction properly forward biased and collector emitter junction properly reverse biased during the application of signal. This can be achieved with a bias battery or associating a circuit with a transistor. The latter method is more efficient and is frequently employed. The circuit which provides transistor biasing is known as *biasing circuit*. It may be noted that transistor biasing is very essential for the proper operation of transistor in any circuit.

should be independent

## 11.4 Stabilisation

The collector current in transistor changes rapidly when :

(i) the temperature changes,

(ii) the transistor is replaced by another of the same type. This is due to the inherent variations of transistor parameters. When the temperature changes or the transistor is replaced, the operating point (i.e. zero signal  $I_C$  and  $V_{CE}$ ) also changes. However, for faithful amplification, it is essential that operating point remains fixed. This necessitates to make the operating point independent of these variations. This is known as stabilisation.

*The process of making operating point independent of temperature changes or variation in transistor parameters is known as stabilisation.*

Once stabilisation is done, the zero signal  $I_C$  and  $V_{CE}$  become independent of temperature variations or replacement of transistor i.e. the operating point is fixed. A good biasing circuit always ensures the stabilisation of operating point.

**Need for stabilisation.** Stabilisation of the operating point is necessary due to the following reasons :—

- (i) Temperature dependence of  $I_C$
- (ii) Individual variations
- (iii) Thermal runaway.

(i) *Temperature dependence of  $I_C$ .* The collector current  $I_B$  is given by ;

$$\begin{aligned} I_C &= \beta I_B + I_{CEO} \\ &= \beta I_B + (\beta + 1) I_{CBO} \end{aligned}$$

The collector leakage current  $I_{CBO}$  is greatly influenced (especially in germanium transistor) by temperature changes. A rise of  $10^\circ\text{C}$  doubles the collector leakage current which may be as high as  $0.2\text{mA}$  for low powered germanium transistors. As biasing conditions in such transistors are generally so set that zero signal  $I_C = 1\text{mA}$ , therefore, the change in  $I_C$  due to temperature variations current cannot be tolerated. This necessitates to stabilise the operating point i.e. to hold  $I_C$  constant inspite of temperature variations.

(ii) *Individual variations.* The value of  $\beta$  and  $V_{BE}$  are not exactly the same for any two transistors even of the same type. Further,  $V_{BE}$  itself decreases when temperature increases. When a transistor is replaced by another of the same type, these variations change the operating point. This necessitates to stabilise the operating point i.e. to hold  $I_C$  constant irrespective of individual variations in transistor parameters.

(iii) *Thermal runaway.* The flow of collector current produces heat within the transistor. This raises the transistor temperature and if no stabilisation is done, the collector leakage current also increases. The increased collector leakage current further raises the transistor temperature. This rise in temperature further increases the collector leakage current. In this way, in a matter of seconds, the collector current may become very large, thus destroying the transistor.

*The self-destruction of an unstabilised transistor is known as thermal runaway.*

In order to avoid thermal runaway and consequent destruction of transistor, it is very important that operating point is stabilised.

### 11.5 Essentials of a transistor biasing circuit

It has already been discussed that transistor biasing is required for faithful amplification. The biasing network associated with the transistor should meet the following requirements :

- (i) It should ensure proper zero signal collector current.
- (ii) It should ensure that  $V_{CE}$  does not fall below 0.5V for Ge transistors and 1V for silicon transistors at any instant.
- (iii) It should ensure the stabilisation of operating point.

### 11.6 Methods of transistor biasing

In the transistor amplifier circuits drawn so far biasing was done with the aid of a battery  $V_{BB}$  which was separate from the battery  $V_{CC}$  used in the output circuit. However, in the interest of simplicity and economy, it is desirable that transistor circuit should have a single source of supply—the one in the output circuit (i.e.  $V_{CC}$ ). The following are the most commonly used methods of obtaining transistor biasing from one source of supply (i.e.  $V_{CC}$ ):

- (i) Base resistor method
- (ii) Biasing with feedback resistor
- (iii) Voltage-divider bias.

In all these methods, the same basic principle is employed i.e. required value of base current (and hence  $I_C$ ) is obtained from  $V_{CC}$  in the zero signal conditions. The value of collector load  $R_C$  is selected keeping in view that  $V_{CE}$  should not fall below 0.5 V for germanium transistors and 1V for silicon transistors.

For example, if  $\beta = 100$  and the zero signal collector current  $I_C$  is to be set at  $1 \text{ mA}$ , then  $I_B$  is made equal to  $I_C/\beta = 1/100 = 10 \mu\text{A}$ . Thus, the biasing network should be so designed that a base current of  $10 \mu\text{A}$  flows in the zero signal conditions.

### 11.7 Base resistor method

In this method, a high resistance  $R_B$  (several hundred  $\text{K}\Omega$ ) is connected between the base and +ve end of supply for *npn* transistor (see Fig. 11.6) and between base and negative end of supply for *pnp* transistor. Here, the required zero signal base current is provided by  $V_{CC}$  and it flows through  $R_B$ . It is because now base is positive *w.r.t.* emitter *i.e.* base-emitter junction is forward biased. The required value of zero signal base current  $I_B$  (and hence  $I_C = \beta I_B$ ) can be made to flow by selecting the proper value of base resistor  $R_B$ .

*Circuit analysis.* It is required to find the value of  $R_B$  so that required collector current flows in the zero signal conditions. Let  $I_C$  be the required zero signal collector current.

$$\therefore I_B = \frac{I_C}{\beta}$$

Considering the closed circuit *ABENA* and applying Kirchhoff's voltage law, we get,

$$V_{CC} = I_B R_B + V_{BE}$$

or

$$I_B R_B = V_{CC} - V_{BE}$$

$\therefore$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} \quad \dots(i)$$

As  $V_{CC}$  and  $I_B$  are known and  $V_{BE}$  can be seen from the transistor manual, therefore, value of  $R_B$  can be readily found from exp. (i).

Since  $V_{BE}$  is generally quite small as compared to  $V_{CC}$ , the former can be neglected with little error. It then follows from exp. (i) that :

$$R_B = \frac{V_{CC}}{I_B}$$

It may be noted that  $V_{CC}$  is a fixed known quantity and  $I_B$  is chosen at some suitable value. Hence,  $R_B$  can always be found directly, and for this reason, this method is sometimes called *fixed-bias method*.

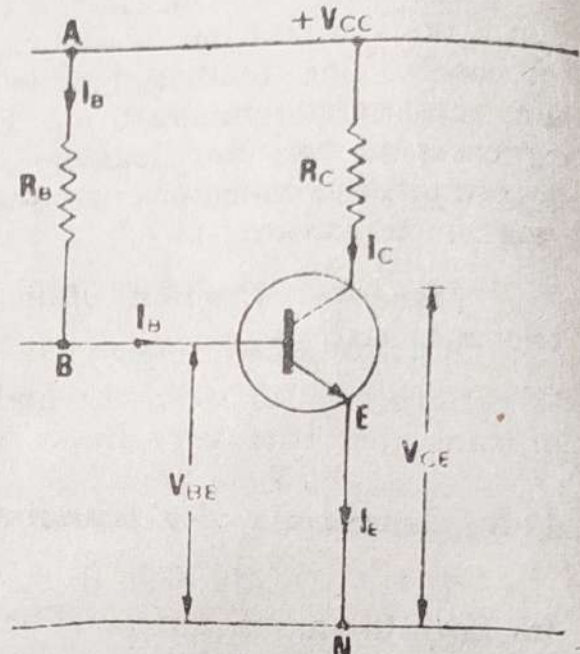


Fig. 11.6

### *Advantages :*

(i) This biasing circuit is very simple as only one resistance  $R_B$  is required.

(ii) Biasing conditions can be easily set and the calculations are simple.

(iii) There is no loading of the source by the biasing circuit since no resistor is employed across base-emitter junction.

### *Disadvantages :*

(i) This method provides poor stabilisation. It is because there is no means to stop a self-increase in collector current due to temperature rise and individual variations. For example, if  $\beta$  increases due to transistor replacement, then  $I_C$  also increases by the same factor as  $I_B$  is constant.

(ii) There are strong chances of thermal runaway.

Due to these disadvantages, this method of biasing is rarely employed.

### 11-8 Biasing with feed back resistor

In this method, one end of  $R_B$  is connected to the base and the other end to the collector as shown in Fig. 11-9. Here, the required zero signal base current is determined *not* by  $V_{CC}$  but by the collector-base voltage  $V_{CB}$ . It is clear that  $V_{CB}$  forward biases the base-emitter junction and hence base current  $I_B$  flows through  $R_B$ . This causes the zero signal collector current to flow in the circuit.

*Circuit analysis.* The required value of  $R_B$  needed to give the zero signal current  $I_C$  can be determined as follows. Referring to Fig. 11-9,

$$V_{CC} = I_C R_C + I_B R_B + V_{BE}$$

$$\text{or } R_B = \frac{V_{CC} - V_{BE} - I_C R_C}{I_B}$$

$$= \frac{V_{CC} - V_{BE} - \beta I_B R_C}{I_B}$$

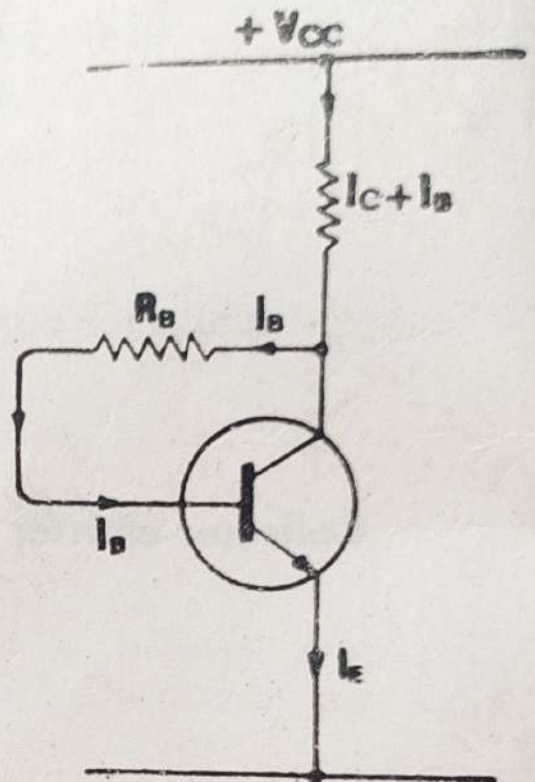


Fig. 11-9

$$(\because I_C = \beta I_B)$$

\*Actually voltage drop across  $R_C = (I_B + I_C) R_C$   
 However,  $I_B \ll I_C$  Therefore, as a reasonable approximation, we can say that drop across  $R_C = I_C R_C$ .

*Advantages :*

- (i) It is a simple method as it requires only one resistance  $R_B$ .
- (ii) This circuit provides some stabilisation of the operating point as discussed below :

Suppose that the temperature increases. This will increase collector leakage current and hence the total collector current. But as soon as the collector current increases,  $V_{CE}$  decreases due to greater drop across  $R_C$ . The result is that lesser voltage is available across  $R_B$ . Hence, the base current decreases. The smaller  $I_B$  tends to decrease the collector current to original value.

*Disadvantages :*

(i) This circuit does not provide good stabilisation. It is because operating point does change, although to lesser extent, due to temperature variations and other effects.

(ii) This circuit provides a negative feed back which reduces the gain of the amplifier as explained hereafter. During the positive half-cycle of the signal, the collector current increases. The increased collector current would result in greater voltage drop across  $R_C$ . This will reduce the base current and hence collector current.

## 12.1 Single stage transistor amplifier

*When only one transistor with associated circuitry is used for amplifying a weak signal, the circuit is known as **single stage transistor amplifier**.*

A single stage transistor amplifier has one transistor, bias circuit and other auxiliary components. Although a practical amplifier consists of a number of stages, yet such a complex circuit can be conveniently split up into separate single stages. By analysing carefully only a single stage and using this single stage analysis repeatedly, we can effectively analyse the complex circuit. It follows, therefore, that single stage amplifier analysis is of great value in understanding the practical amplifier circuits.

## 12.2 How transistor amplifies ?

Fig. 12.1 shows a single stage transistor amplifier. When a weak a.c. signal is given to the base of transistor, a small base current (which is a.c.) starts flowing. Due to transistor action, a much larger ( $\beta$  times the base current) a.c. current flows through



the collector load  $R_C$ . As the value of  $R_C$  is quite high (usually 4–10K $\Omega$ ), therefore, a large voltage appears across  $R_C$ . Thus, a weak signal applied in the base circuit appears in amplified form in the collector circuit. It is in this way that a transistor acts as an amplifier.

The action of transistor amplifier can be beautifully explained by referring to Fig. 12.1. Suppose a change of 0.1V in signal voltage produces a change of 2mA in the collector current. Obviously, a signal of only 0.1V applied to the base will give an output voltage = 2mA  $\times$  5K = 10V. Thus, the transistor has been able to raise the voltage level of the signal from 0.1V to 10V i.e. voltage amplification or stage gain is 100.

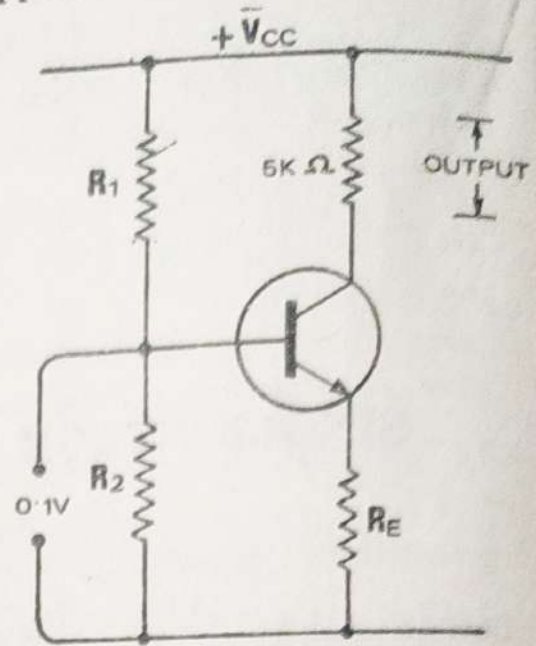


Fig. 12.1

### 12.3 Graphical demonstration of transistor amplifier

The function of transistor as an amplifier can also be explained graphically. Fig. 12.2 shows the output characteristics of a transistor in  $CE$  configuration. Suppose the zero signal base current is  $10\mu A$  i.e. this is the base current for which the transistor is biased by the biasing network. When an a.c. signal is applied to the base, it makes the base, say positive in the first half-cycle and, negative in the second half-cycle. Therefore, the base and collector currents will increase in the first half-cycle when base-emitter junction is more forward-biased. However, they will decrease in the second half-cycle when the base-emitter junction is less forward biased.

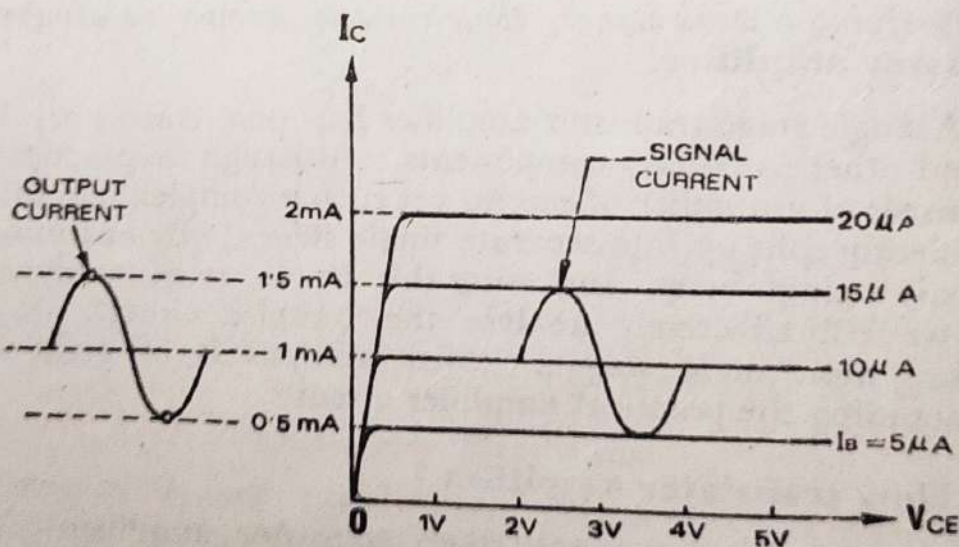


Fig. 12.2

For example, consider a sinusoidal signal which increases or decreases the base current by  $5\mu A$  in the two half-cycles of the signal. Referring to Fig. 12.2, it is clear that in the absence of signal, the base current is  $10\mu A$  and the collector current is  $1mA$ .

However, when the signal is applied in the base circuit, the base current and hence collector current change continuously. In the first half-cycle peak of the signal, the base current increases to  $15\mu A$  and the corresponding collector current is  $1.5mA$ . In the second half-cycle peak, the base current is reduced to  $5\mu A$  and the corresponding collector current is  $0.5mA$ . For other values of the signal, the collector current is in between these values *i.e.*  $1.5mA$  and  $0.5mA$ .

It is clear from Fig. 12.2 that  $10\mu A$  base current variations result in  $1mA$  ( $1,000\mu A$ ) collector current variations *i.e.* by a factor of 100. This large change in collector current flows through collector resistance  $R_C$ . The result is that output signal is much larger than the input signal. Thus, the transistor has done amplification.

#### 12.4 Practical circuit of transistor amplifier

It is important to note that a transistor can accomplish faithful amplification only if proper associated circuitry is used with it. Fig. 12.3 shows a practical single stage transistor amplifier. The various circuit elements and their functions are described below :

(i) *Biasing circuit.* The resistances  $R_1$ ,  $R_2$  and  $R_E$  form the biasing and stabilisation circuit. The biasing circuit must establish a proper operating point otherwise a part of the negative half-cycle of the signal may be cut off in the output,

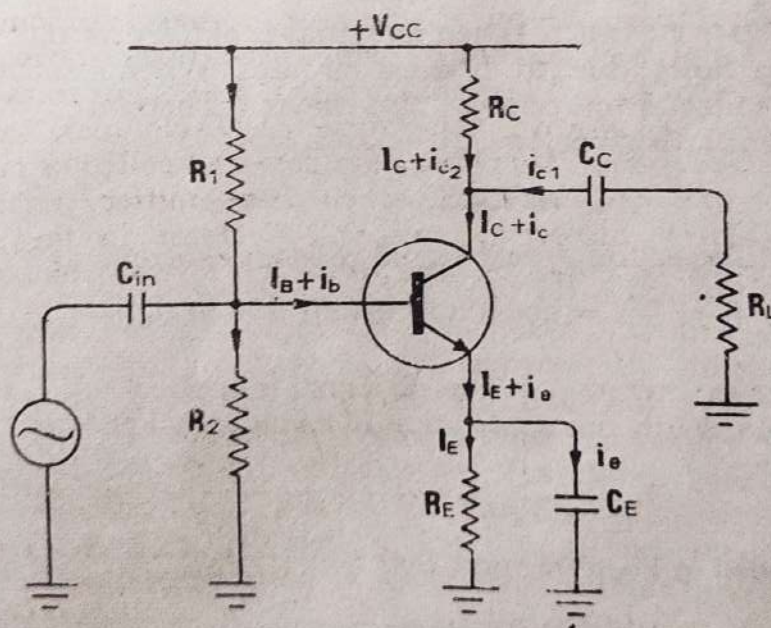


Fig. 12.3

(ii) *Input capacitor  $C_{in}$ .* An electrolytic capacitor  $C_{in}$  ( $\approx 10\mu f$ ) is used to couple the signal to the base of the transistor. If it is not used, the signal source resistance will come across  $R_2$  and thus change the bias. The capacitor  $C_{in}$  allows only a.c. signal to flow but isolates the signal source from  $R_2$ .\*

\*It may be noted that a capacitor offers infinite reactance to d.c. and blocks it completely whereas it allows a.c. to pass through it.

However, when the signal is applied in the base circuit, the base current and hence collector current change continuously. In the first half-cycle peak of the signal, the base current increases to  $15\mu A$  and the corresponding collector current is  $1.5mA$ . In the second half-cycle peak, the base current is reduced to  $5\mu A$  and the corresponding collector current is  $0.5mA$ . For other values of the signal, the collector current is in between these values *i.e.*  $1.5mA$  and  $0.5mA$ .

It is clear from Fig. 12.2 that  $10\mu A$  base current variations result in  $1mA$  ( $1,000\mu A$ ) collector current variations *i.e.* by a factor of 100. This large change in collector current flows through collector resistance  $R_C$ . The result is that output signal is much larger than the input signal. Thus, the transistor has done amplification.

#### 12.4 Practical circuit of transistor amplifier

It is important to note that a transistor can accomplish faithful amplification only if proper associated circuitry is used with it. Fig. 12.3 shows a practical single stage transistor amplifier. The various circuit elements and their functions are described below :

(i) *Biasing circuit.* The resistances  $R_1$ ,  $R_2$  and  $R_E$  form the biasing and stabilisation circuit. The biasing circuit must establish a proper operating point otherwise a part of the negative half-cycle of the signal may be cut off in the output.

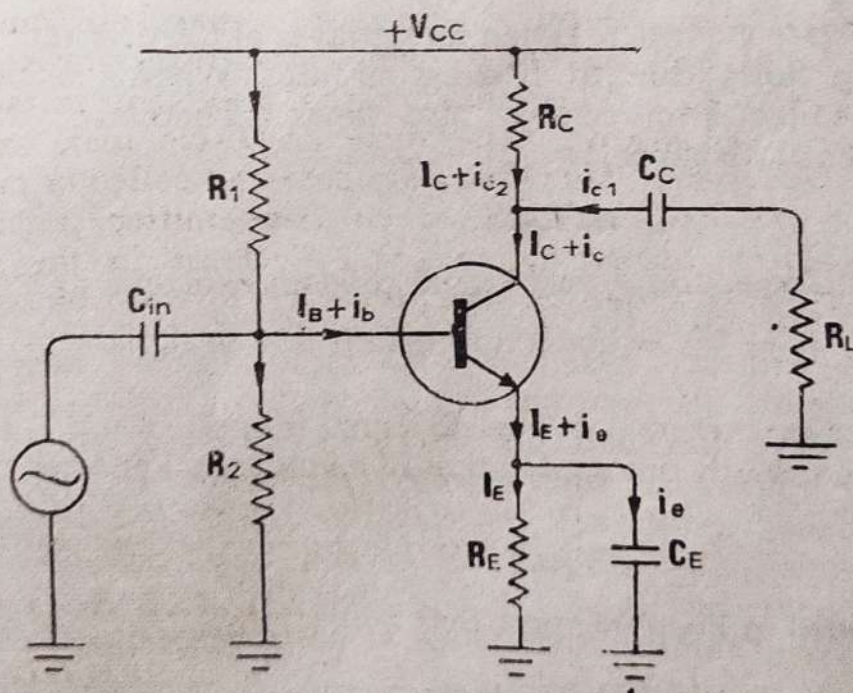


Fig. 12.3

(ii) *Input capacitor  $C_{in}$ .* An electrolytic capacitor  $C_{in}$  ( $\approx 10\mu f$ ) is used to couple the signal to the base of the transistor. If it is not used, the signal source resistance will come across  $R_2$  and thus change the bias. The capacitor  $C_{in}$  allows only a.c. signal to flow but isolates the signal source from  $R_2$ .\*

\*It may be noted that a capacitor offers infinite reactance to d.c. and blocks it completely whereas it allows a.c. to pass through it.

(iii) *Emitter bypass capacitor*  $C_E$ . An emitter bypass capacitor  $C_E$  ( $\approx 100\mu F$ ) is used in parallel with  $R_E$  to provide a low reactance path to the amplified a.c. signal. If it is not used, then amplified a.c. signal flowing through  $R_E$  will cause a voltage drop across it, thereby reducing the output voltage.

(iv) *Coupling capacitor*  $C_C$ . The coupling capacitor  $C_C$  ( $\approx 10\mu F$ ) couples one stage of amplification to the next stage. If it is not used, the bias conditions of the next stage will be drastically changed due to the shunting effect of  $R_C$ . This is because  $R_C$  will come in parallel with the upper resistance  $R_1$  of the biasing network of the next stage, thereby altering the biasing conditions of the latter. In short, the coupling capacitor  $C_C$  isolates the d.c. of one stage from the next stage, but allows the passage of a.c. signal.

**Various circuit currents.** It is useful to mention the various currents in the complete amplifier circuit. These are shown in the circuit of Fig. 12.3.

(i) *Base current.* When no signal is applied in the base circuit, a d.c. base current  $I_B$  flows due to biasing circuit. When a.c. signal is applied, a.c. base current  $i_b$  also flows. Therefore, with the application of signal, total base current  $i_B$  is given by ;

$$i_B = I_B + i_b$$

(ii) *Collector current.* When no signal is applied, a d.c. collector current  $I_C$  flows due to biasing circuit. When a.c. signal is applied, a.c. collector current  $i_c$  also flows. Therefore, the total collector current  $i_C$  is given by ;

$$i_C = I_C + i_c$$

where  $I_C = \beta I_B =$  zero signal collector current

$i_c = \beta i_b =$  collector current due to signal.

(iii) *Emitter current.* When no signal is applied, a d.c. emitter current  $I_E$  flows. With the application of signal, total emitter current  $i_E$  is given by ;

$$i_E = I_E + i_e$$

It is useful to keep in mind that :

$$I_E = I_B + I_C$$

$$i_e = i_b + i_c$$

Now base current is usually very small, therefore, as a reasonable approximation,

$$I_E \approx I_C \quad \text{and} \quad i_e \approx i_c$$